

Cpr E 281 HW03

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

NAND/NOR Gates with Synthesis Minimization and Karnaugh Maps

Assigned: Week 4

Due Date: Feb. 12, 2023

P1 (12 points): Given the expression $G(W, X, Y, Z) = \sum m(0, 1, 3, 7, 8, 15)$, implement this function using no more than 8 NAND gates. The NAND gates that you use may have any number of inputs. You may not use NOT gates to create this circuit.

P2 (16 points): Given the expression $H(A, B, C) = \sum m(0, 1, 5, 7)$, perform the following:

- Write the expression for H as a simplified SOP expression.
- Write the expression for H as a simplified POS expression.
- Implement H using exactly five NOR gates and no other gates.
- Did you use the SOP expression or the POS expression to implement the circuit? Why?

P3 (9 points): Produce the simplified sum-of-products (SOP) expressions for the following K-maps:

BC	00	01	11	10
A				
0	1	1	0	0
1	1	1	0	0

YZ	00	01	11	10
WX				
00	1	0	0	1
01	1	1	0	0
11	1	1	0	0
10	0	0	0	0

YZ	00	01	11	10
WX				
00	0	0	0	0
01	0	1	0	0
11	1	0	0	0
10	1	0	0	1

P4 (21 points): For each shorthand expression below, derive the simplest SOP expression:

A: $F_1(w, x, y, z) = \sum m(4, 6, 10, 11, 14, 15)$

B: $F_2(x, y, z) = \sum m(2, 5, 6, 7)$

C: $F_3(w, x, y, z) = \sum m(0, 2, 3, 7, 8, 10, 11, 15)$

P5 (21 points): For each expression below, derive the simplest POS expression:

A: $G_1(a, b, c, d) = \prod M(0, 1, 2, 3, 4, 5, 10, 11)$

B: $G_2(a, b, c) = \prod M(0, 2, 3, 6)$

C: $G_3(a, b, c, d) = \prod M(0, 2, 5, 9, 13)$

P6 (21 points): Use Karnaugh Maps to convert the following expressions to simplified SOP expressions:

I: $H_1(A, B, C, D) = \bar{C}D + B\bar{C} + BCD + AC\bar{D} + A\bar{B}C$

II: $H_2(A, B, C, D) = (A + C + D)(B + C + \bar{D})(\bar{A} + B + \bar{C})$

III: $H_3(A, B, C, D) = \prod M(0, 2)$

P1) $G = (W, X, Y, Z) = \sum m(0, 1, 3, 7, 8, 15)$


* using no more than 8 NAND gates & no NOR gates

6

		yz				
wx			00	01	11	10
00			0	1	3	2
01			4	5	7	6
11			12	13	15	14
10			8	9	11	10

$$G = \overline{X}\overline{Y}\overline{Z} + \overline{W}\overline{X}Z + XYZ$$

W X Y Z

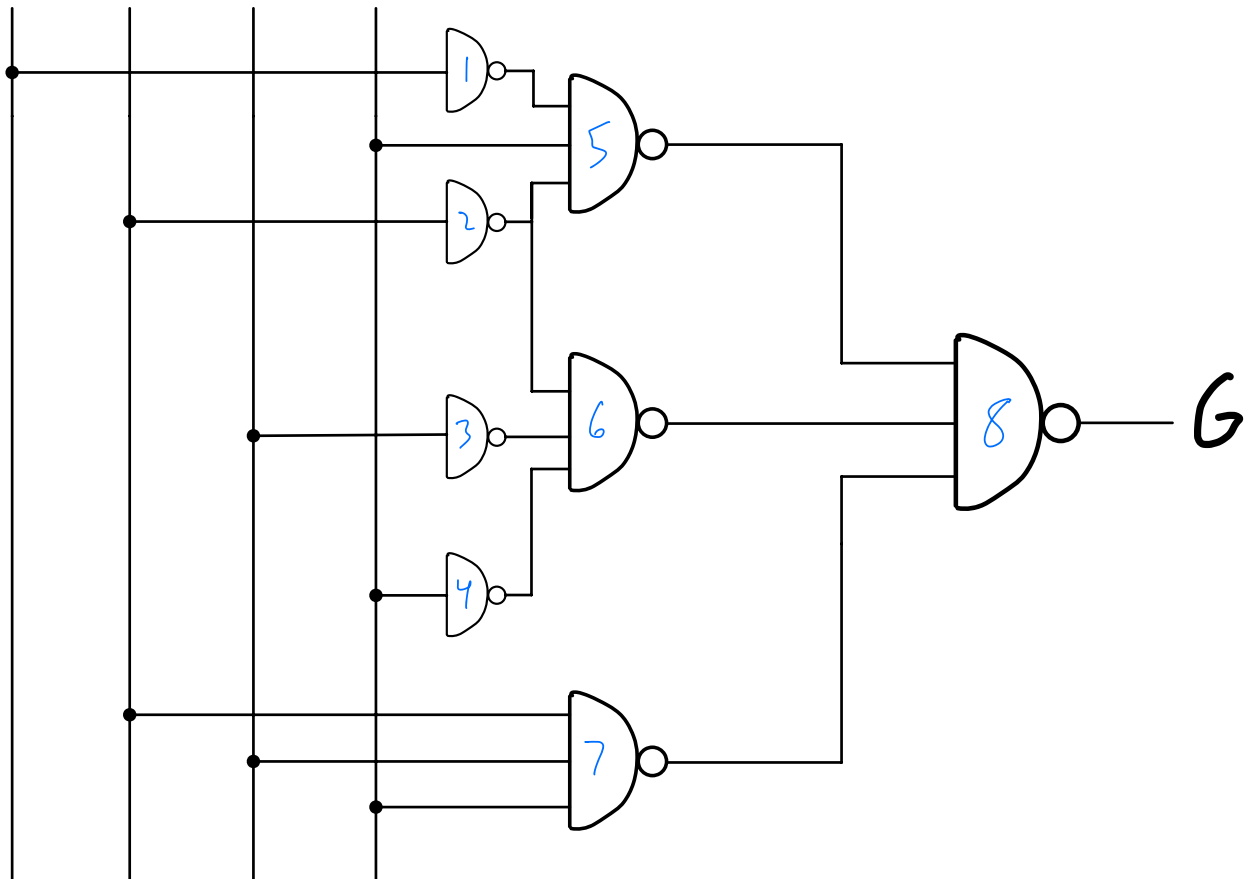

P2) $H(A, B, C) = \sum m(0, 1, 5, 7)$


a) Simplified SOP | b) Simplified POS | c) Implement using NOR | d) POS or why? SOP?

H

	ab		
	00	01	11
c	0	1	2
0	1	1	0
1	0	1	1
	4	5	6

a) $\bar{a}\bar{b} + ac$ SOP

b) $(a + \bar{b})(\bar{a} + c)$ POS

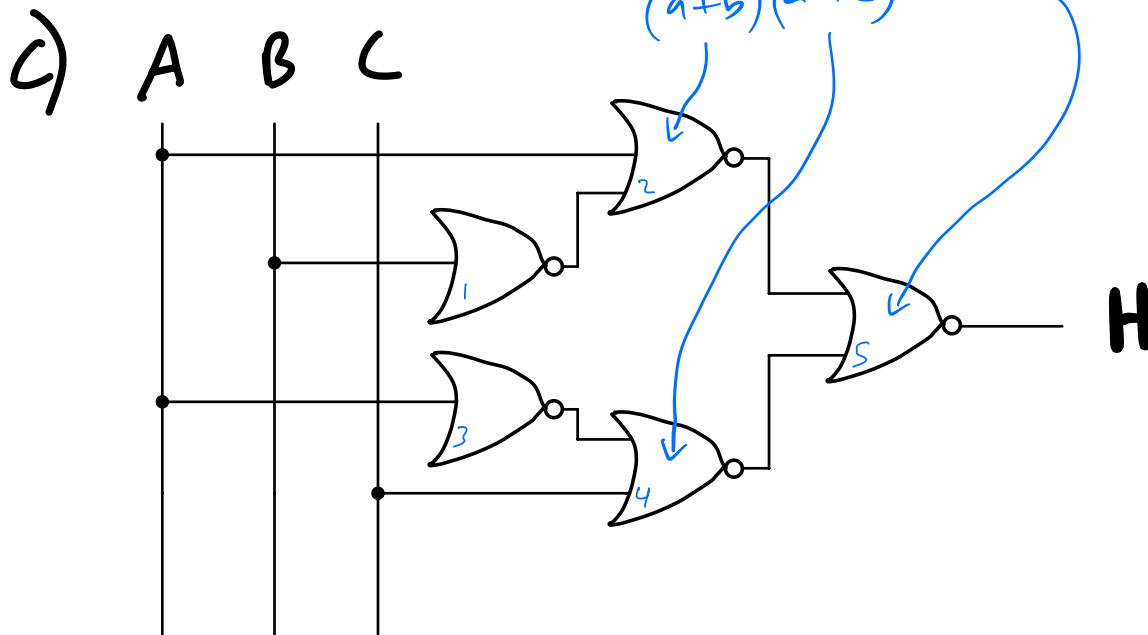

d) POS is far easier to implement using NOR gates compared to SOP, as shown above, $\Rightarrow \overline{(a+b)(a+c)}$

P3) 1)

A \ BC	00	01	11	10
	0	1	0	0
0	1	1	0	0
1	1	1	0	0

$$= \overline{B}$$

2)

WX \ YZ	00	01	11	10
	0	1	0	1
00	1	0	0	1
01	1	1	0	0
11	1	1	0	0
10	0	0	0	0

$$= (X \overline{Y}) + (\overline{W} \overline{X} \overline{Z})$$

3)

WX \ YZ	00	01	11	10
	0	1	0	1
00	0	0	0	0
01	0	1	0	0
11	1	0	0	0
10	1	0	0	1

$$= (W \overline{Y} \overline{Z}) + (W \overline{X} \overline{Z}) + (\overline{W} X \overline{Y} Z)$$

P4) A) $F_1(w, x, y, z) = \sum m(4, 6, 10, 11, 14, 15)$

SOP B) $F_2(x, y, z) = \sum m(2, 5, 6, 7)$

C) $F_3(w, x, y, z) = \sum m(0, 2, 3, 7, 8, 10, 11, 15)$

A) F_1

w\y\z	y\z			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$= (\overline{w} \overline{x} y) + (\overline{w} x \overline{z}) + (x y \overline{z})$$

B) F_2

x\y\z	y\z			
	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$= (x z) + (y \overline{z})$$

C) F_3

w\y\z	y\z			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

3 groups

$$= (\overline{x} y) + (\overline{x} \overline{z}) + (\overline{w} y z)$$

P5) A) $G_1(a, b, c, d) = \prod M(0, 1, 2, 3, 4, 5, 10, 11)$

POS B) $G_2(a, b, c) = \prod M(0, 2, 3, 6)$

C) $G_3(a, b, c, d) = \prod M(0, 2, 5, 9, 13)$

A) G_1

	cd	00	01	11	10
ab	00	0	0	0	0
	01	0	0	1	1
	11	1	1	1	1
	10	1	1	0	0

$= \sum m(6, 7, 8, 9, 12, 13, 14, 15)$ SOP
2 groups POS

$= (a+c)(b+\bar{c})$

B) G_2

	cd	00	01	11	10
ab	00	0	1	0	0
	01	1	1	1	1
	11	1	1	1	0

$= \sum m(1, 4, 5, 7)$ SOP
3 groups POS

$= (a+\bar{b})(a+c)(\bar{b}+c)$

C) G_3

	cd	00	01	11	10
ab	00	0	1	1	0
	01	1	0	1	1
	11	1	0	1	1
	10	1	0	1	1

$= \sum m(1, 3, 4, 6, 7, 8, 10, 11, 12, 14, 15)$ SOP
3 groups POS
Cannot group 3

$= (a+b+d)(\bar{a}+c+\bar{d})(\bar{b}+c+\bar{d})$

P6) Use K MAPS to convert to simplified SOP expressions

I) $H_1(A, B, C, D) = \bar{C}D + B\bar{C} + BC\bar{D} + AC\bar{D} + A\bar{B}C$

II) $H_2(A, B, C, D) = (A + C + D)(B + C + \bar{D})(\bar{A} + B + \bar{C})$

III) $H_3(A, B, C, D) = \prod M(0, 2)$

I) H_1

5 groups
SOP

	cd	00	01	11	10
ab	00	0	1		3
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$\bar{C}D = (1, 5, 9, 13)$ $B\bar{C} = (4, 5, 12, 13)$ $AC\bar{D} = (10, 14)$
 $BC\bar{D} = (6, 14)$ $A\bar{B}C = (10, 11)$

$\Sigma m(1, 4, 5, 6, 9, 10, 11, 12, 13, 14) = \text{SOP } H_1 =$
 $= \bar{B}\bar{C} + B\bar{D} + C\bar{D} + A\bar{B}C$

reduces to only 4 groups

II) H_2

POS
3 groups

	cd	00	01	11	10
ab	00	X	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$\text{POS } H_2 = \Sigma M(4, 5, 6, 11, 14, 15)$
 $\text{SOP } H_2 = \Sigma m(1, 2, 3, 7, 8, 9, 10, 13, 14)$

4 SOP groups =

$\text{SOP } H_2 =$
 $A\bar{C} + \bar{A}\bar{B}D + \bar{B}C\bar{D} + CD\bar{A}$

$A + C + D = (11, 15)$
 $B + C + D = (6, 14)$
 $\bar{A} + B + \bar{C} = (4, 5)$

III) H_3

$\prod M(0, 2) = \Sigma m(1, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16)$

reduces to 3 SOP groups

$\text{SOP } H_3(A, B, C, D) =$
 $A + B + D$

	cd	00	01	11	10
ab	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10