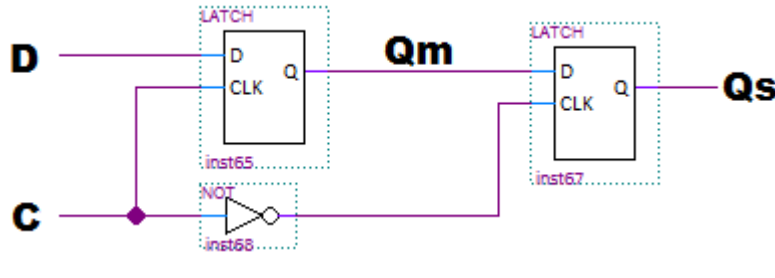


Cpr E 281 HW07
ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY


Representation and Arithmetic
Assigned: Week 10

P1. (20 points): Answer the following questions based on the circuit shown below.



| clk | D | Q |
|-----|---|---|
| 0 | 0 | X |
| 0 | 1 | X |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

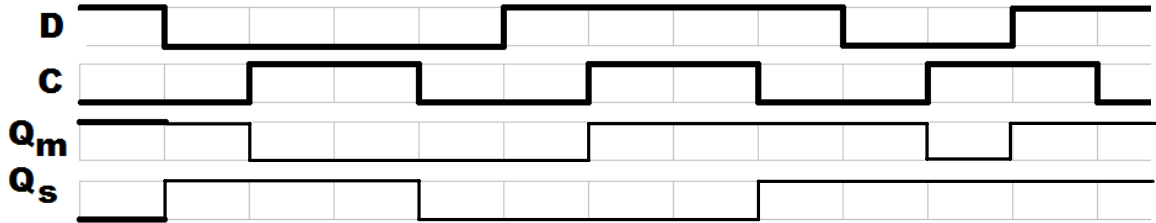- A.** A: The latch that appears (twice) in the above circuit is a D Latch. Show the characteristic table for a D Latch.
- B.** B: Fill in the timing diagram for the values shown above.




P2. (10 points): Show how a D Flip-Flop (DFF) can be made using a T Flip-Flop (TFF). Your circuit must contain all of the functionality of a DFF (PRESET and CLEAR implementations are not necessary), but must use only one TFF and one 2-1 MUX.

P3. (30 points): We want to create an LM-latch with the characteristic table shown below:

| L | M | Q | P |
|---|---|-----------|-----------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | No change | No change |
| 1 | 0 | No change | No change |
| 1 | 1 | 1 | 0 |

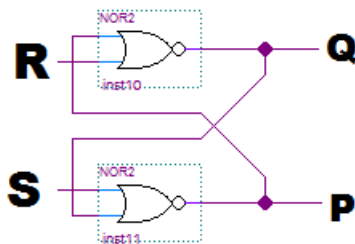A. Show the characteristic table for the SR Latch shown below.




| S | R | Q | P |
|---|---|--------|--------|
| 0 | 0 | Memory | Memory |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

B. For each input combination to the LM-latch characteristic table shown above, write the values of S and R that will produce the output combinations. Then derive expressions for S and R in terms of L and M.


C. Draw the completed circuit for the LM-latch with the characteristic table based on the expressions derived in part B.

P4. (40 points): Complete the following timing diagrams for the specified components. The clock is C. You may assume that Q is initially at 0 unless specified otherwise.

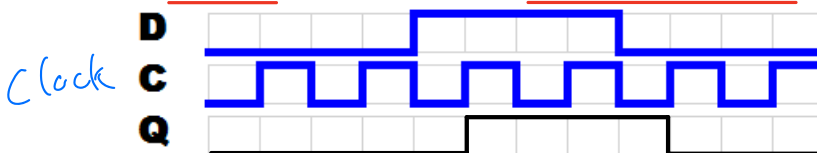
A. A positive-edge-triggered D Flip-Flop (DFF).



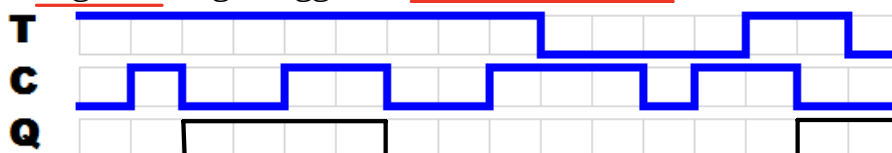
B. A negative-edge-triggered T Flip-Flop (TFF).



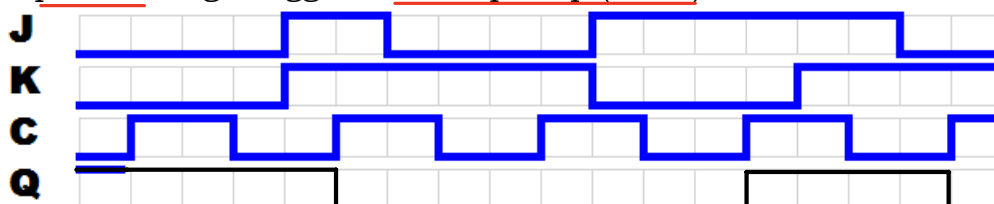C. A positive-edge-triggered JK Flip-Flop (JKFF).



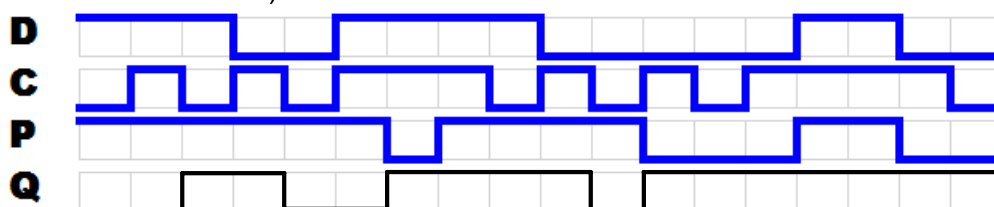
D. A negative-edge-triggered DFF with active-low Preset P (preset occurs when P=0).



P2)

0 0 0 0
0 1 0 1
1 0 1 1
1 1 1 0

T Flip Flop

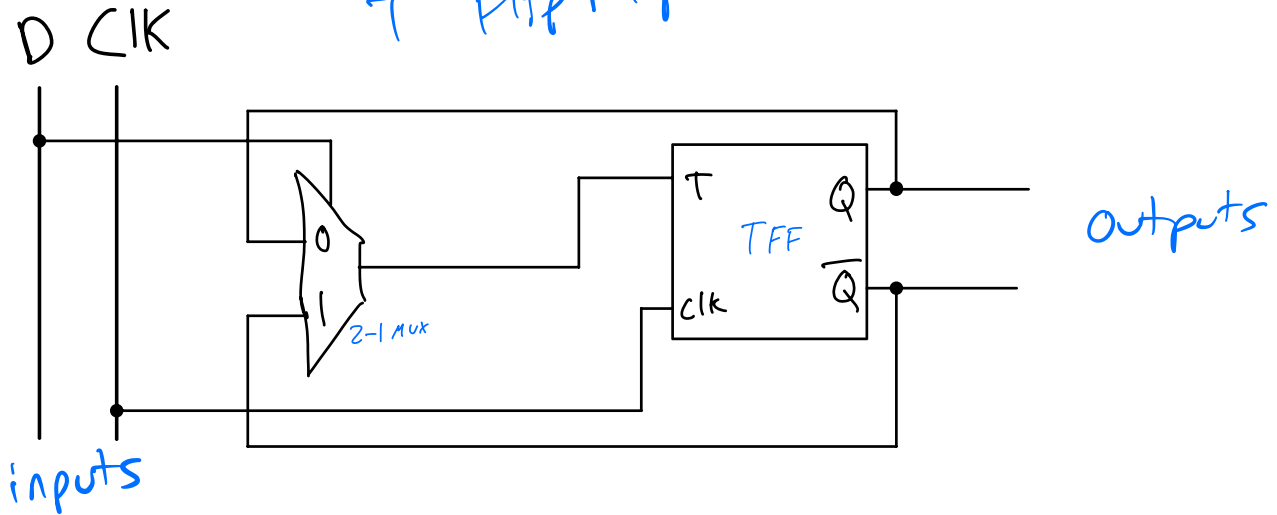

P3)

Lm Latch

| L | M | S | R | Q | P |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | X | X |
| 1 | 0 | 0 | 0 | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 |

