

### Instructions

Complete the question below to the best of your ability. Once complete, upload a PDF of your work to canvas.

### Questions

**P1. Decoder Synthesis (2 x 25p each = 50p)**

**a) (25p)** Draw the truth table for the function  $f(X, Y, Z) = \bar{X}Y + \bar{X}Z + X\bar{Y}\bar{Z}$

**b) (25p)** Implement  $f$  using one 3-to-8 decoder and a minimal number of gates.

a)


X	Y	Z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

X \ YZ	00	01	11	10
0	0	1	1	1
1	1	0	0	0

$$\bar{X}Y + \bar{X}Z + X\bar{Y}\bar{Z}$$

$$f(X, Y, Z) = \sum m(1, 2, 3, 4)$$

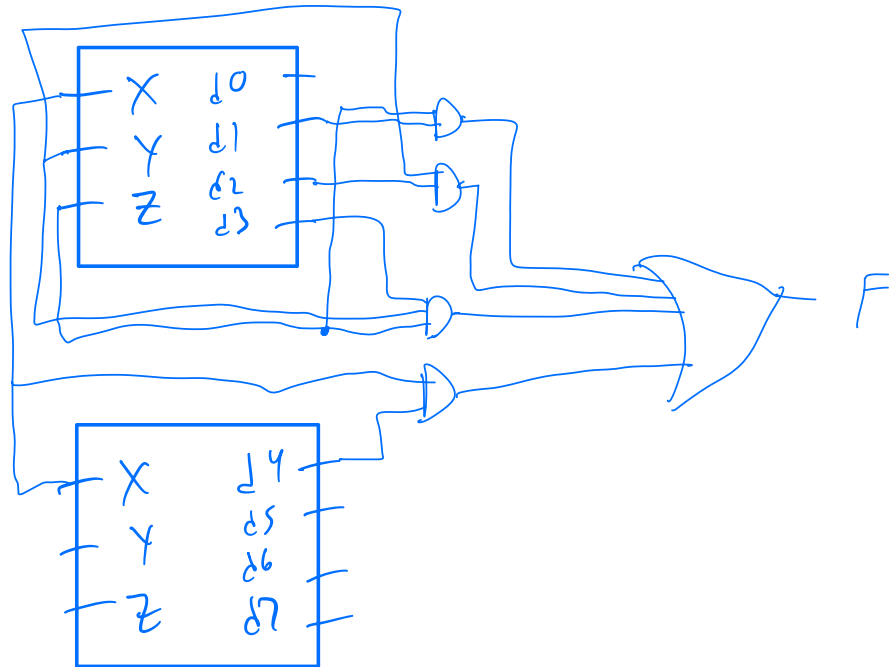b) implement F using 3 to 8 decoder + minimum gates



inputs				out puts							
	X	Y	Z		$Z \cdot d1$	$Y \cdot d2$	$Y \cdot Z \cdot d3$	$X \cdot d4$			
F	X	Y	Z	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	0	0	0	1	0
0	1	1	1	0	0	0	0	0	0	0	1