

Instructions

Complete the question below to the best of your ability. Once complete, upload a PDF of your work to canvas.

Questions

P1. (20 points) Implement the function $f(x_1, x_2, x_3) = \prod M(0, 1, 2)$ using only NOR gates. [Consider minimal cost implementation]

P2. (20 points) Implement the function $f(x_1, x_2, x_3) = \prod M(0, 1, 5, 6, 7)$ using only NAND gates. [Consider minimal cost implementation]

(P1)

$$f(x_1, x_2, x_3) = \prod M(0, 1, 2) \text{ using NOR}$$

$$f = (\bar{x}_1 + x_2)(\bar{x}_1 + \bar{x}_3)$$

$x_2 x_3$

	00	01	11	10
x_1 0	0	0		0
1				

x_1	x_2	x_3

$x_1 + x_2$

$\overline{x_1 + x_3}$

$\overline{\overline{x_1 + x_2} + \overline{x_1 + x_3}}$

f


$F = (x_1 + x_2)(x_1 + x_3)$

$$f = (x_1 + x_2)(x_1 + x_3)$$

P2 $f(x_1, x_2, x_3) = \prod M(0, 1, 5, 6, 7)$ using NAND

$$f = (\overline{x_1} + \overline{x_2})(x_2 + \overline{x_3})$$
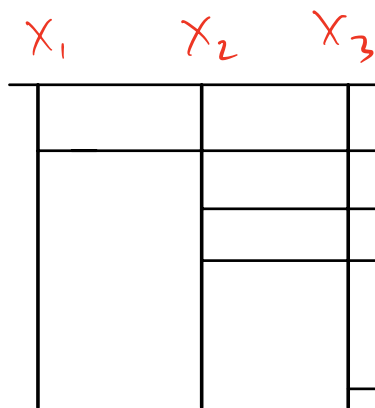
$$f = \overline{x_1} x_2 + \overline{x_2} \overline{x_3}$$



$x_2 x_3$

	00	01	11	10
x_1 0	1	0	1	1
x_1 1	1	0	0	0

$$\overline{x_1} x_2 + \overline{x_2} \overline{x_3}$$

$$f = \overline{x_1} x_2 + \overline{x_2} \overline{x_3}$$