

CprE 281 QUIZ 7

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Initial Stuff and Basics

Assigned Date: Week # 10



Instructions

Complete the question below to the best of your ability. Once complete, upload a PDF of your work to canvas.

  Questions

P1. Timing Diagram (1x 20p each = 30p)

Assume that Q is initially zero for this problem. Complete the timing diagram for a gated D Latch shown below:



P2. D flip-flop (1 x 10p each = 10p)


Draw a circuit diagram of the positive-edge-triggered D flip-flop with synchronous preset.

below

P3. Timing Diagram (1x 20p each = 30p)

Assume that Q is initially zero for this problem. Complete the timing diagram for a negative edge-triggered T flip-flop shown below:


T flip flop

 

P4. Timing Diagram (1x 20p each = 30p)

Assume that Q is initially zero for this problem. Complete the timing diagram for a positive edge-triggered J-K flip-flop shown below:

J-K flip flop

 

P2) inputs

synchronous d
 preset | |

